Hardware Design Explanation and Part Justification

This circuit board integrates power regulation, signal control, sensing, and communication, making it suitable for high-power embedded systems. At its core is the STM32F103C8Tx microcontroller, supported by components for stable power, robust protection, and reliable connectivity. The PCB layout includes power planes to ensure thermal and electrical stability under high-load conditions.

1. Microcontroller Section

The STM32F103C8Tx ARM Cortex-M3 microcontroller is selected for its low power consumption and built-in peripherals (I²C, UART, PWM, USB). Operating at 3.3V, it is supported by multiple 100nF decoupling capacitors to reduce noise. A 16 MHz crystal (Y1) and 10pF capacitors provide accurate timing essential for USB and communication protocols.

2. Power Supply and Regulation

This section converts a 36V input to a stable 3.3V output:

- AP63205WU Buck Converter (U2) efficiently steps down the voltage using internal MOSFETs to minimize heat.
- \cdot L1 (4.7 μH) and C14–C16 (22 μF) form a low-ripple output filter. Extra capacitors (100nF, 1 μF) ensure noise suppression.
- Q1 (P-MOS) offers reverse polarity protection, preventing damage from incorrect power input.

3. Protection Elements

The design includes protection against voltage surges and electrical noise:

- TVS Diodes (D4, D6) protect power and signal lines from transient spikes.
- Ferrite Bead (FB1) reduces high-frequency EMI, improving signal integrity.
- Snubber Diode (D3) handles voltage spikes from inductive loads.
- **R6 and SW1** implement a soft-start mechanism, reducing inrush current and allowing manual enable control.

4. Power Plane and Layout Considerations

To manage high currents and minimize heat:

- Dedicated 3.3V and GND Planes allow even current distribution and low resistance paths.
- Thermal Reliefs around components like U2, Q2, and U3 aid in heat dissipation through ground pours and vias.

- 3.3VA and 3.3V Grounds are separated to isolate analog sensors from digital noise.
- · Mounting Holes and Ground Pads support mechanical stability and EMI reduction.

5. High-Power Switching & Motor Control

- · IRF7483M (Q2), an N-channel MOSFET, handles switching of high-current loads efficiently. It's driven by PWM signals and supports fast switching.
- **IR2110 (U3)** is a gate driver that boosts MCU PWM signals to suitable gate levels and includes built-in protections like shoot-through prevention.

6. Sensor and Communication Interfaces

- NTC Thermistor Input (J12) allows temperature sensing via an external sensor, connected through jumpers.
- · I²C and UART Headers (J8, J9) support interfacing with external modules. Pull-ups (R2, R4) are present for I²C.
- · USB Micro-B (J5) enables communication or programming, with TVS protection on data lines.

7. General Purpose and Miscellaneous Elements

- · D1 LED and R8 provide visual power indication.
- · SWD Header allows in-system debugging and flashing.
- · SW1 and BOOT0 configure the microcontroller boot mode.
- · PWR_FLAGs and labeled test points facilitate simulation and hardware testing in KiCad.